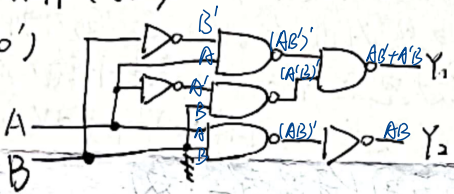


二. 计算 (50')

1. (10')



(1) Y_1, Y_2 最简与或表达式 (4')

(2) 真值表 (3')

(3) 分析, 判断逻辑功能 (3')

(1) $Y_1 = AB' + A'B$

$Y_2 = AB$


(2) 真值表

A	B	Y_1	Y_2
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

(3) Y_1 实现了异或运算

Y_2 实现了与运算

2. (15') 双四选一数据选择器构成电路

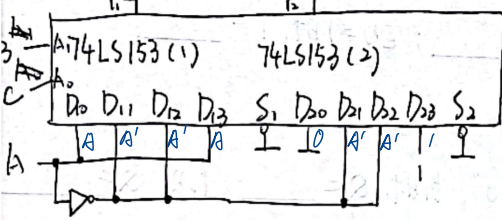

(1) 列真值表, 写出 Y_1, Y_2 逻辑函数表达式

(最小项之和形式) (6')

(2) 分析, 判断逻辑功能 (3')

(3) 在 74HC138 译码器图中用 74HC138 与门重现功能

3. (15') 用边沿触发的 JK 触发器设计电路


(1)

A	B	C	Y_1	Y_2
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$Y_1 = A(B'C' + BC) + A'(B'C + BC') = A \oplus B \oplus C$

$Y_2 = A'B'C + A'BC' + A'BC + ABC$
 $= \sum m(1, 2, 3, 7)$


001
010
011
111

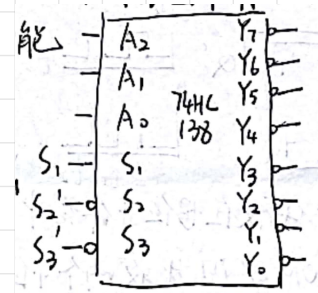

3. (15') 用负边沿触发的JK触发器设计电路 (16')

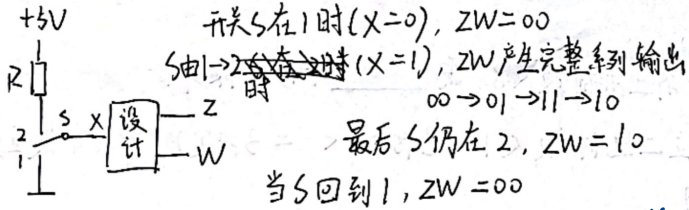

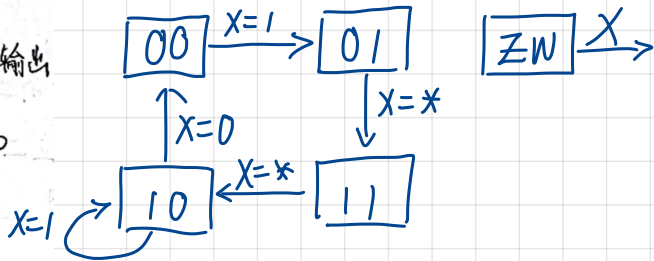- (1) 画出电路最简状态转换图 (4')
- (2) 画出次态卡诺图, 化简 (4')
- (3) 状态方程, 驱动方程, 输出方程 (5')
- (4) 画逻辑电路图 (2')



(2)

	ZW	00	01	11	10
X	0		✓	✓	
	1		✓	✓	✓

XZ

Z^*

	ZW	00	01	11	10
X	0		✓		
	1	✓	✓		

W^*

$$Z^* = (W + XZ) = WZ' + (W + X)Z$$

$$W^* = XZ' + Z'W$$

$$= XZ'(W' + W) + Z'W$$


$$= XZ'W' + Z'W$$

$$J_1 = W$$


$$J_2 = XZ'$$

$$K_1 = (W + X)'$$

$$K_2 = Z$$

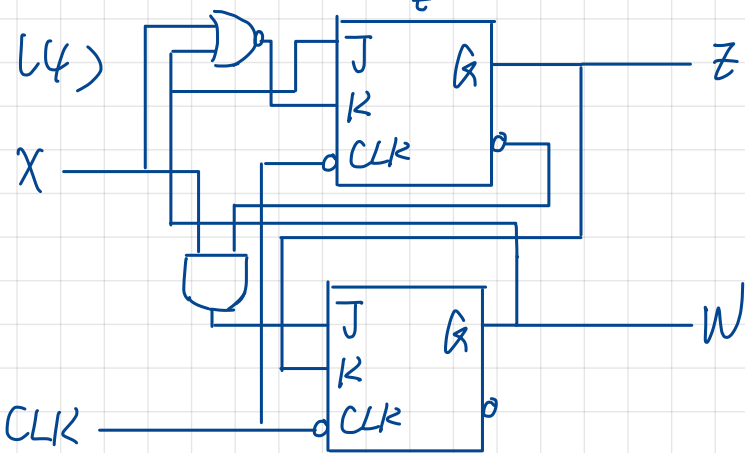

4. (10') 3个JK触发器 (TTL) 初始状态为0.

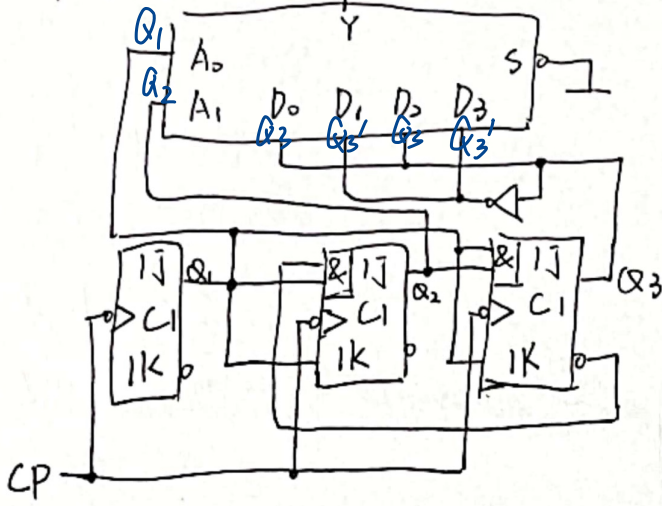

(1) 驱动方程, 状态方程 (6')

(2) 画出状态转换图 (3')

(3) 在时序电路的输出控制下, 数据选择器的输出序列 (1')

$$J_1 = K_1 = 1 \quad \text{状: } Q_1^* = Q_1'$$


$$J_2 = Q_1 Q_3' \quad K_2 = Q_1$$

$$J_3 = Q_1 Q_2 \quad K_3 = Q_1$$

$$Q_2^* = Q_1 Q_3' Q_2' + Q_1' Q_2 = Q_3' Q_2' Q_1 + Q_2 Q_1'$$

$$Q_3^* = Q_1 Q_2 Q_3' + Q_1' Q_3 = Q_3' Q_2 Q_1 + Q_3 Q_1'$$

(2)

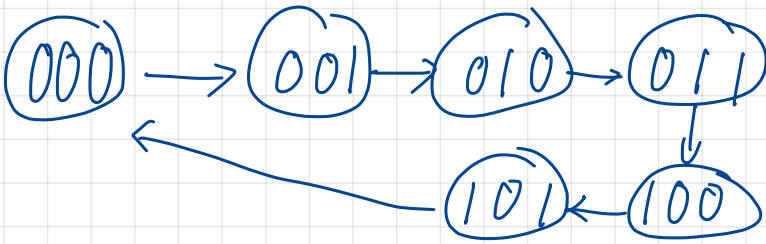

(3)

	$Q_3 Q_2 Q_1$	Y
1	000	0
2	001	1
3	010	0
4	011	1
5	100	1
6	101	0
7	000	0