

二、(15分)

蓝笔为分析，不用写在试卷上

基础题。

①  $G_1 G_0 = 00$ ;  $A_2 A_1 A_0 = 00A$ ,

A	B	Y
0	0	0 (=D <sub>0</sub> )
0	1	0 (=D <sub>0</sub> )
1	0	1 (=D <sub>1</sub> )
1	1	1 (=D <sub>1</sub> )

$\Rightarrow Y = AB' + AB = A$

②

$G_1 G_0 = 01$ ;  $A_2 A_1 A_0 = 01A$ ,

A	B	Y
0	0	0 (=D <sub>2</sub> = B)
0	1	1 (=D <sub>2</sub> )
1	0	1 (=D <sub>3</sub> = B')
1	1	0 (=D <sub>3</sub> )

$\Rightarrow Y = A'B + AB' = A \oplus B$

③

$G_1 G_0 = 10$ ;  $A_2 A_1 A_0 = 10A$ ,

A	B	Y
0	0	0 (=D <sub>4</sub> )
0	1	0 (=D <sub>4</sub> )
1	0	0 (=D <sub>5</sub> = B)
1	1	1 (=D <sub>5</sub> )

$\Rightarrow Y = AB$

④

$G_1 G_0 = 11$ ;  $A_2 A_1 A_0 = 11A$ ,

A	B	Y
0	0	0 (=D <sub>6</sub> = B)
0	1	1 (=D <sub>6</sub> )
1	0	1 (=D <sub>7</sub> = B')
1	1	0 (=D <sub>7</sub> )

$\Rightarrow Y = A'B + AB' = A \oplus B$

三、(15分)

(1) 所有触发器的时钟输入均为同一CLK, 则为同步时序逻辑。

(2)  $Y_1 = \sum m(0, 3, 6) = Q_2' Q_1' Q_0' + Q_2' Q_1 Q_0 + Q_2 Q_1 Q_0'$

$Y_2 = \sum m(0, 2, 4, 7) = Q_2' Q_1' Q_0' + Q_2' Q_1 Q_0' + Q_2' Q_1 Q_0 + Q_2 Q_1 Q_0 = Q_1' Q_0' + Q_2' Q_1 Q_0' + Q_2 Q_1 Q_0$

(3) 驱动方程:  $J_0 = K_0 = Q_2(Q_1 \oplus Q_0)$      $J_1 = K_1 = 1$      $J_2 = Q_0 + Q_1$      $K_2 = Q_0 \oplus Q_1$

状态方程

$Q_0^* = J_0 Q_0' + K_0' Q_0 = Q_0' [Q_2(Q_1' Q_0' + Q_1 Q_0)] + Q_0 [Q_2' + Q_1 \oplus Q_0] = \sum m(1, 3, 4, 5)$

$Q_1^* = Q_1'$


$Q_2^* = J_2 Q_2' + K_2' Q_2 = (Q_0 + Q_1) Q_2' + (Q_0 \oplus Q_1) Q_2 = Q_0 Q_2' + Q_1 Q_2' + Q_0 Q_1' Q_2 + Q_0' Q_1 Q_2 = \sum m(1, 2, 3, 5, 6)$

主要是细心耐心,

个人感觉还不错。

	$Q_1 Q_0$			
$Q_2$	00	01	11	10
0	0	1	1	1
1	0	1	0	1

	$Q_1 Q_0$			
$Q_2$	00	01	11	10
0	0	1	1	0
1	1	1	0	0

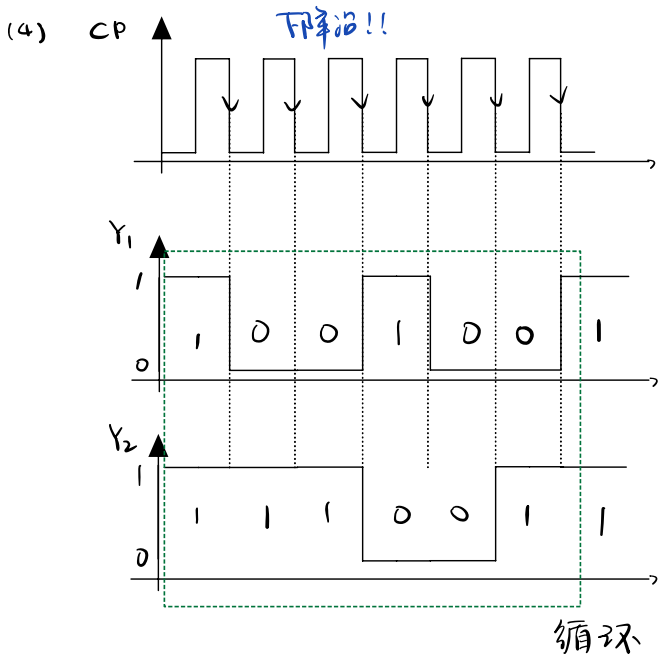

	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>
0	0	0	0	1	1
2	0	1	0	0	1
4	1	0	0	0	1
3	0	1	1	1	0
5	1	0	1	0	0
7	1	1	1	0	1
0	0	0	0	1	1
1	0	0	1	0	0
7	1	1	1	0	1
6	1	1	0	1	0
4	1	0	0	0	1

(5) 为六进制计数器、