

## 6. 4A 1A (注意单位)

[解析] 该两个线性电阻网络组成的复合二端口的 A 参数为  $A = \begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix}$

$$\text{则 } U_S = A_{11}U'_1 - A_{12}I'_2 \quad \text{结合实际电路知 } U'_1 = I_3R_3, I'_2 = -I_3, \text{ 再代入数据得 } \begin{cases} 9 = 3A_{11} + A_{12} \\ 10 = 2A_{12} \end{cases} \quad \text{得 } \begin{cases} A_{11} = \frac{4}{3} \\ A_{12} = 5\Omega \end{cases}$$

$$\text{当 } U_S = 13V, R_3 = 6\Omega \text{ 时, } I'_2 = -I_3, U'_1 = 6I_3 \quad \text{得 } 13 = (8+5)I_3 \quad \Rightarrow I_3 = 1A$$

再设右侧二端口的 A 参数为  $A^b = \begin{bmatrix} A_{11}^b & A_{12}^b \\ A_{21}^b & A_{22}^b \end{bmatrix}$  则  $I_2 = A_{21}^b U'_1 - A_{22}^b I'_2$ , 结合实际电路知  $U'_1 = I_3R_3, I'_2 = -I_3$ ,

$$\text{再代入数据得 } \begin{cases} 3 = 3A_{21}^b + A_{22}^b \\ 4 = 2A_{22}^b \end{cases} \quad \text{得 } \begin{cases} A_{21}^b = \frac{1}{3} \\ A_{22}^b = 2 \end{cases} \quad \text{当 } U_S = 13V, R_3 = 6\Omega \text{ 时, 已求得 } I_3 = 1A, \text{ 则得 } I_2 = \frac{1}{3} \times 6 \times 1 - (-1) \times 2 = 4A$$

7. 解: 由已参数得  $\begin{cases} U_1 = 4\bar{i}_1 + 2\bar{i}_2 & (\text{参考方向如图}) \\ U_2 = 3\bar{i}_1 + 4\bar{i}_2 \end{cases}$

又由二端口网络右侧二端口接 2Ω 电阻, 有  $U_2 = -2\bar{i}_2$


$$\text{得 } -6\bar{i}_2 = 3\bar{i}_1 \Rightarrow U_1 = 4\bar{i}_1 - \bar{i}_1 = 3\Omega \quad \Rightarrow R_{in} = 3\Omega$$

$$\text{开关闭合前 } \bar{i}_L(0-) = \frac{6}{4.5}A = \frac{4}{3}A \quad \text{由换路定律 } \bar{i}_L(0+) = \frac{4}{3}A$$

$$\text{从电感视入的等效电阻 } R_{eq} = 4\Omega \quad \Rightarrow T = \frac{L}{R} = 0.025s$$

$$\bar{i}_L(\infty) = \frac{6V}{1.5\Omega + 3\Omega // 3\Omega} \times \frac{1.5\Omega}{3\Omega} = 1A \quad \Rightarrow \text{由三要素公式得 } \bar{i}_L(t) = 1 + \frac{1}{3} e^{-40t}, t > 0$$
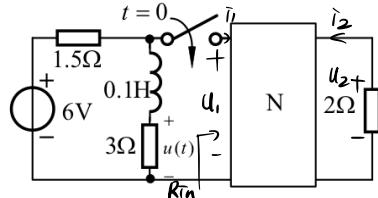
$$\therefore U(t) = 3\bar{i}_L(t) = 3 + e^{-40t}, t > 0, \quad f(t) = f_p(t) + [f(0^+) - f_p(0^+)]e^{-t/T} \xrightarrow{\text{若有稳态}} f(0) + [f(0^+) - f(0)]e^{-t/T}.$$



8. 波从一端传播到另一端的时间  $t = \frac{L}{V} = \frac{3 \times 10^{-4}}{3 \times 10^8} s = 10^{-4}s = 100\mu s$

在  $0 \sim 100\mu s$  时, 从右端发出的入射波到达终端,  $U^+ = 20kV, I^+ = 50A$ ,

$$\therefore U^+(x,t) = 20 \varepsilon(t - \frac{x}{3 \times 10^8}) kV, I^+(x,t) = 50 \varepsilon(t - \frac{x}{3 \times 10^8}) A$$

$100\mu s$  时, 入射波到达终端, 发生反射。由于终端接一般性负载, 故用波阻抗法分析其量值。

画出其集中参数等效电路图如右所示:


$$T = \frac{L}{R} = 2 \times 10^{-7}s \quad U(0+) = 2U^+ = 40kV \quad (\text{零状态电感相当于开路})$$

$$U(\infty) = \frac{100}{100+400} \times 2U^+ = 8kV \quad \therefore U(t) = 8 + 32e^{-5 \times 10^6 (t - 10^{-4}s)} \quad \text{因 } U(t) = U^+(t) + U^-(t), \text{ 由 } V \text{ 得}$$

$$\text{电压反向行波 } U^-(x,t) = [-12 + 32e^{-5 \times 10^6 (t - 10^{-4}s)}] \varepsilon(t - 2 \times 10^{-4} + \frac{x}{3 \times 10^8}) \quad (kV)$$

$$\text{电流反向行波 } I^-(x,t) = \frac{U^-(t)}{Z_C} = [-30 + 80e^{-5 \times 10^6 (t - 10^{-4}s)}] \varepsilon(t - 2 \times 10^{-4} + \frac{x}{3 \times 10^8}) \quad (A)$$

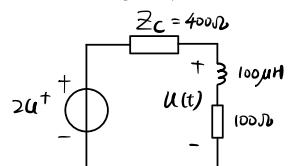$\therefore t = 150\mu s$  时, 传输线上电压电流分布为



$$u(x,t) = 20 \varepsilon(t - \frac{x}{3 \times 10^8}) + [-12 + 32 e^{-5 \times 10^6 (t - 10^{-4} s)}] \varepsilon(t - 2 \times 10^{-4} + \frac{x}{3 \times 10^8}) \text{ (kV)} \quad [V \text{ 为始端为零点}]$$

$$= 20 + [-12 + 32 e^{-5 \times 10^6 (t - 10^{-4} s)}] \varepsilon(t - 2 \times 10^{-4} + \frac{x}{3 \times 10^8}) \text{ (kV)}$$

$$i(x,t) = 50 \varepsilon(t - \frac{x}{3 \times 10^8}) - [-30 + 80 e^{-5 \times 10^6 (t - 10^{-4} s)}] \varepsilon(t - 2 \times 10^{-4} + \frac{x}{3 \times 10^8}) \text{ (A)} \quad [V \text{ 为始端为零点}]$$

$$= 50 - [-30 + 80 e^{-5 \times 10^6 (t - 10^{-4} s)}] \varepsilon(t - 2 \times 10^{-4} + \frac{x}{3 \times 10^8}) \text{ (A)}$$

(注: 不少分析单向线左右两岸是分析, 因为上述阶跃函数中代入  $t = 150 \mu s$  即可知有一半传播线还没有反向行波)

9. 解: 当电源直流量单独作用时, 电感相当于短路, 把电阻忽略掉了, 电压表上无压降,

所以电压表读数即为电源交流分量单独作用时, 电感或右侧电阻上电压有效值.

而此时电感的感抗为  $Z_L = j0.5 \Omega$ ,  $\therefore$  电感上电流有效值  $I_L = 2A$ , 电阻上电流有效值  $I_R = 1A$

$\therefore$  流过电流表总电流有效值  $I_{(1)} = \sqrt{2^2 + 1} = \sqrt{5} A$  (电压有效值与电流有效值之比等于阻抗摸)

$\therefore$  当直流量单独作用时电流有效值  $I_{(0)} = \sqrt{3^2 - (\sqrt{3})^2} = 2A$

设  $N$  的待求参数矩阵为  $A = \begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix}$

当直流量单独作用时,  $U_S = A_{11} U_2' - A_{12} I_2'$  ( $U_2'$ 、 $I_2'$  为二端口右端电压电流)

$$U_2' = 0, \quad I_2' = -2A, \quad U_S = 8V, \quad \therefore A_{12} = 4\Omega$$

(参考方向)

电源交流分量单独作用时, 则  $U_S = A_{11} U_2' - A_{12} I_2'$  ( $U_2'$ 、 $I_2'$  为二端口右端电压电流)

设  $I_R = 1\angle 0^\circ A$ ,  $I_L = -2j\angle 90^\circ A$ ,  $U_2' = I_R$ ,  $I_2' = -(I_L + I_R)$  又  $U_S = 8\sqrt{2}\angle 0^\circ V$ , 有

$$8\sqrt{2}\angle 0^\circ = A_{11} I_R + 4(1-2j) I_R \quad \text{得} \quad 8\sqrt{2}\angle 0^\circ = [(A_{11} + 4) - 8j] I_R$$

由模关系可知:  $128 = 64 + (A_{11} + 4)^2$  得  $A_{11} = -12$  (舍去)  $A_{11} = 4$  从而  $I_R = 1\angle 45^\circ A$ .

当电感、电阻串联时, 当直流量单独作用时, 电感相当于短路,

$$\therefore \delta = 4 \times I_{R(0)} + 4 \times I_{R(1)} \quad \therefore I_{R(1)} = 1A, \quad U_{R(0)} = 1V$$

电源交流分量单独作用时, 由 A 参考方程得  $8\sqrt{2} = 4 \times (\dot{I}_{R(1)} + j0.5 \times \dot{I}_{R(1)}) + 4 \times \dot{I}_{R(1)}$

$$\therefore 8\sqrt{2} = (8+2j) \dot{I}_{R(1)} \quad \text{由此有} \quad I_{(1)} = \dot{I}_{R(1)} = \frac{8\sqrt{2}}{2\sqrt{17}} = \frac{4\sqrt{34}}{17} A$$

$$U_{(2)} = (1+0.5j) \frac{8\sqrt{2}}{8+2j} \quad \text{又} \quad U_{(2)} = \frac{8\sqrt{2}}{2\sqrt{17}} \times \frac{\sqrt{5}}{2} = \frac{2\sqrt{10}}{\sqrt{17}} V$$

$$\therefore I = \sqrt{I^2 + (\frac{4\sqrt{34}}{17})^2} = 1.698 A \quad U = \sqrt{I^2 + (\frac{2\sqrt{10}}{\sqrt{17}})^2} = 1.831 V$$

5. [解] (1) 经端匹配时, 线上各处电压相量与电流相量比值为  $Z_C$ , 则入端电压  $\dot{U}_{in} = \frac{\dot{U}_{sm}}{Z_C + R_i} = 50\angle 0^\circ V$

$$\text{电流 } \dot{I}_{in} = 1\angle 0^\circ A \quad \Rightarrow \text{线上电压的相量表达式为 } \dot{U}_n(x) = \dot{U}_{in} \cos \beta x - j Z_C \dot{I}_{in} \sin \beta x = 50 \cos 2\pi x - j 50 \sin 2\pi x$$

$$\text{时域表达式为 } u(x, t) = 50 \cos \omega t \cos 2\pi x - 50 \cos(\omega t + \frac{\pi}{2}) \sin 2\pi x = 50 \cos \omega t \cos 2\pi x + 50 \sin \omega t \sin 2\pi x$$

$$\text{同理, } i(x, t) = \cos(\omega t - 2\pi x).$$

$$(2) \text{ 因终端短路, 则 } Z_L = j Z_C \tan \beta l = j \times 50 \times \tan \frac{2\pi}{l} \times 3.25 = \infty$$

$$\Rightarrow U_{in} = U_m = 100\angle 0^\circ V \quad I_m = 0$$

$$\therefore \text{相量形式的线间电压电流表达式} \quad \begin{cases} \dot{U}_n(x) = 100 \cos \beta x = 100 \cos(2\pi x) \\ \dot{I}_m(x) = -2j \sin \beta x = -2j \sin(2\pi x) \end{cases}$$

$$\therefore \text{转化为时域表达式为 } u(x, t) = 100 \cos(2\pi x) \cos(\omega t),$$

$$i(x, t) = 2 \sin(2\pi x) \cos(\omega t - \frac{\pi}{2}).$$